



## IS1200/IS1500

### ***Lab 4 – Processor Design*** ***2017-01-17***

## Introduction

Welcome to this lab! In this laboratory exercise, you will learn the fundamentals of processor design. After finishing this lab, you should be able to

1. Construct a simple single-cycle processor that executes a real assembly program.
2. Explain how bit selection and instruction decoding works.
3. Explain the basic principles of the data path and the control unit.

## Preparations

You must do the lab work in advance, except for the Surprise Assignment. The teachers will examine your skills and knowledge at the lab session.

We recommend that you book a lab-session well in advance, and start preparing at least a week before the session.

You can ask for help anytime before the lab session. There are several ways to get help; see the course website for details and alternatives. We especially encourage you to post questions on KTH social.

During the lab session, the teachers work with examination as well as offering help. Make sure to state clearly that you want to *ask questions*, rather than being examined.

Sometimes, our teachers may have to refer help-seekers to other sources of information, so that other students can be examined.

## Software

In this lab, we use the the open source software **Logisim**. You can download and install the software from <http://cburch.com/logisim/>. If you have not performed the LD-Lab, you need to learn the basics of using this software before you do Lab 4.

To teach yourself how to use the Logisim tool, please go through Logisim's "Beginner's tutorial". You can find the tutorial in the documentation section on Logisim's webpages. Note that you need to perform each of the steps by using the software, so that you really learn how to use the tool.

If you are taking course IS1200, you should already know the basics of digital design and the content of the LD-Lab (Logic Design), that is only examined for students taking IS1500. However, if you find Lab 4 a bit hard, we recommend that you perform at least parts of the LD-Lab to refresh your knowledge about digital design.

## Resources and Reading Guidelines

- Lectures 9.
- Harris & Harris (2013) course book. Chapters 5.2.4 (about the ALU), and 7.1, 7.3 (about the single-cycle processor). The book is available online.
- The MIPS Reference Sheet.
- See the course web page *Literature and Resources* for links and details.

## Examination

Examination is divided into three parts:

Part 1 – Assignments 1 and 2.

Part 2 – Assignments 3 and 4.

Part 3 – Assignments 5 and 6 (the surprise).

Examining one part takes between 5 to 15 minutes. Make sure to call the teacher immediately when you are done with an assignment.

Please state clearly that you want to *be examined*, rather than getting help.

The teacher checks that your solution behaves correctly, and that your solution follows all coding requirements and is easily readable.

The teacher will also ask questions, to check that your knowledge of the design and implementation of your solution is deep, detailed, and complete. When you create your solution, do not forget to make detailed notes. With these notes, you can quickly refresh your memory during examination, if some particular detail has slipped your mind.

You must be able to answer all questions. In the unlikely case that some of your answers are incorrect or incomplete, we follow a specific procedure for re-examination.

# Assignments

Through-out all assignments, test your components carefully by trying different input data and check the output against expected output.

NOTE! Before you start, download file **processor.circ** from the course website. This is the template project in which you should implement *all* your solutions. Open this file in Logisim and start your processor design journey!

## Assignment 1: Arithmetic/Logical Unit (ALU)

The ALU is the heart of the processor and is the digital building block that performs the actual computations. The purpose of this assignment is to get a deeper understanding of how an ALU can be designed, by implementing a basic ALU. The ALU is very similar to the one presented at Lecture 9, with one extension (see below).

### Task 1.1

Open circuit ALU in the **processor.circ** project. Implement the ALU with the following properties:

- One 32-bit wide data input port named A.
- One 32-bit wide data input port named B.
- One 3-bit input port named F that determines the function of the ALU.
- One 32-bit data output port named Y that outputs the result of the selected function.
- One 1-bit output port named Zero that output value 1 if all bits of Y is zero else it outputs value 0.


Note that the input and output components and some other help components are already located in the **ALU** circuit.

The ALU should implement the following functionality.

- $F = 000_2$  should perform operation A AND B.
- $F = 001_2$  should perform operation A OR B.
- $F = 010_2$  should perform operation A + B.
- $F = 110_2$  should perform operation A - B.
- $F = 111_2$  should perform operation *set less than (SLT)*. That is, if  $A < B$  then the ALU should output value 1, else it should output value 0.

For all other values of F, the output is undefined (we do not care what the output is).

 When the ALU circuit is used in another circuit, the layout will look like this.



The layout for the component is already provided in the project.

**Please note:** For this lab, you are not allowed to use the Subtractor component in Logisim. All the other pre-defined components are allowed.

Some advice:

- Input pins and output pins can be configured to be 32-bit. Note, however, that the most significant byte is displayed at the top and the least significant byte at the bottom. Take a look at Example 1 in circuit **Tests** (part of the project) and convince yourself of the bit structure.
- The ALU is very similar to the one that is presented in Harris & Harris in Section 5.2.4, as well as the one presented in Lecture 9. Note however the new **Zero** output port, which must be defined using Logisim components of your choice.
- One option to perform the zero extension (for the SLT operation) is to nest two *Splitter* components to extract the sign bit, followed by a *Bit Extender* component, which can be found in the *Wire* library folder. As an alternative, use the **Bit Selector** component that can be found in the **Plexers** library folder. You can also take a look at examples 2 and 3 in the **Tests** circuit.

### Questions for Assignment 1

These questions are useful to prepare yourself for the oral examination. However, at the examination, the teacher may choose to ask questions that are not on this list.

- Explain how each of the ALU functions are defined. In particular, you need to be able to explain how subtraction works, including the use of two's complement.
- How did you implement the logic for the **Zero** output port? Did you consider any alternatives? Be prepared to explain your design choices.
- What is the purpose of the ALU? Why are several functions grouped together into one component?

### Assignment 2: Register File

In this assignment, you will implement a register file with 2 read ports and 1 write port. The register file will then later be used to store the register values for the processor. This register file will only be able to handle the first 8 registers (\$0, \$at, \$v0, \$v1, \$a0, \$a1, \$a2, and \$a3). All registers are 32-bit. We do this simplification to avoid that the circuits get too complex.

In circuit **RegisterFile**, an almost complete 3-bit addressed register file is provided.

#### Task 2.1

Register \$0 (also called \$Zero) has a special semantics. Implement the correct behavior for \$0 in the circuit.

#### Task 2.2

For debugging purposes in later assignments, it is convenient to output the value for register \$v0. Add connections to the circuit so that register \$v0 is sent to output port **v0**.

## Questions for Assignment 2

These questions are useful to prepare yourself for the oral examination. However, at the examination, the teacher may choose to ask questions that are not on this list.

- Explain if the read operation or the write operation, or both operations are clocked (updated at the clock edge). Why is it implemented this way?
- Explain the semantics of reading from and writing to \$0, and how you implemented this behavior.
- How many bits of data can this register file store? If the address width was the same size as for a complete 32-bits MIPS processor, how many bits would in such a case such register file store?

## Assignment 3: Control Unit

In this assignment you will implement a small control unit. You need to have a good understand of both the control unit and the data path for the single-cycle processor, as presented at the lectures and in the course book. Note also that this control unit is a simplified version of the unit presented at the lectures and in the book; it cannot handle all instructions.

Circuit **Control Unit** is prepared with correct (but not optimal) implementation that can handle instructions **addi** and **add**.


### Task 3.1

Add logic and components to circuit **ControlUnit** so that it can also handle the correct control signals for instruction **beq**.
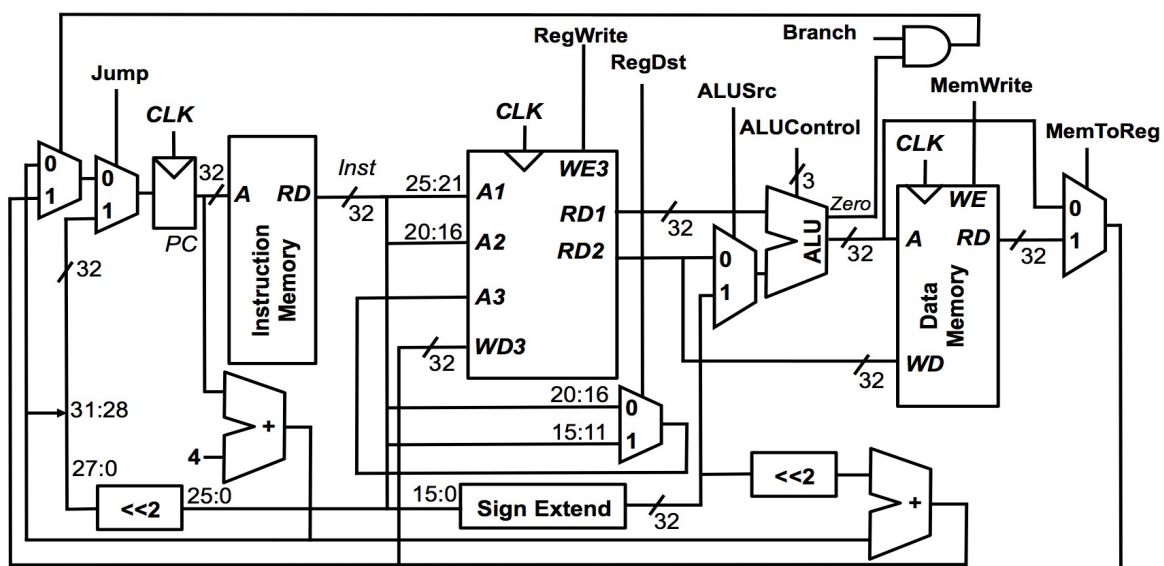
## Questions for Assignment 3

These questions are useful to prepare yourself for the oral examination. However, at the examination, the teacher may choose to ask questions that are not on this list.

- Explain how you have implemented the control signals for the **beq** instruction. Why is this a correct solution?
- Be prepared to explain why the RegDst control signal or the ALUSrc signal is hooked up to certain signals. You should be prepared to explain this using the following figure.



## Assignment 4: Data path


In this task, you should create a data path that can handle three MIPS instructions correctly: instructions **addi**, **add**, and **beq**. This is the most demanding assignment in this lab, so follow the instructions below carefully. It is very important that you verify each of the instructions using the supplied test program.

### Task 4.1: Updating the program counter and fetching instructions

1. Go to the **Datapath** circuit. All components in this assignment should be added to this circuit.
2. The circuit already contains the register for the PC counter and the connection to the instruction memory. Add logic for incrementing the PC with value 4 (next instruction). Note that the address width of the program counter is 8 bits, so that we do not need to allocate a too big ROM memory. Test the circuit with the provided clock.
3. The code memory should be implemented using the read-only memory (ROM) component in Logisim (under library director Memory). This component is already provided in the **Datapath** circuit. The address bit width is 8 bits and the data bit width 32 bits. Note also that we have added a shift component before the ROM address input (shift right by 2) so that the PC address corresponds to extracting one word (4 bytes). Initiate it and test that you can fetch instructions after each other. To see that it works correctly, it is good to add an output port, that you can for observing output during testing.

### Task 4.2: Implementing the addi instruction.

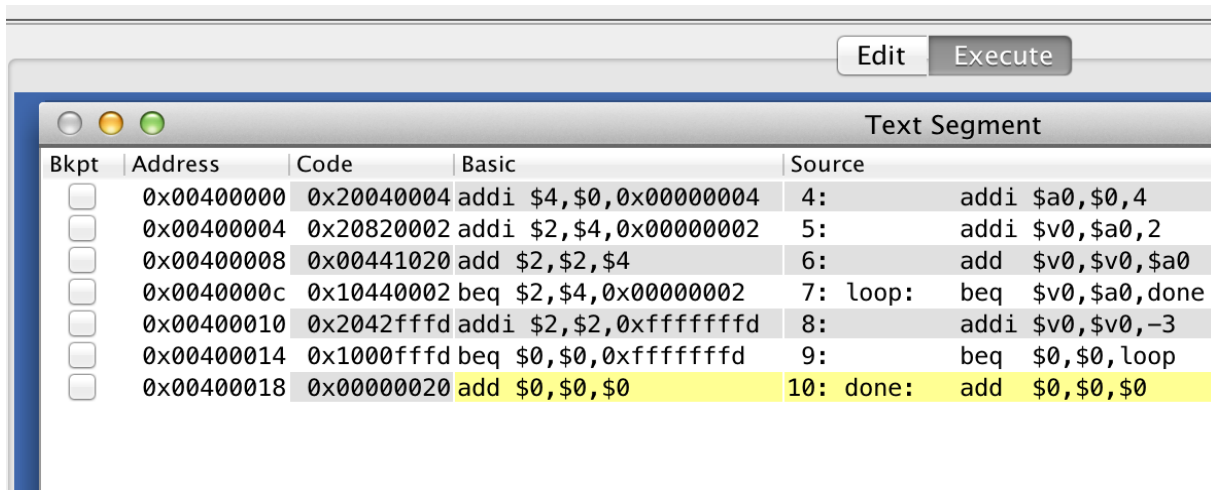
1. The first thing to do is to create a test program that we can use to see that the operation works. Download the program **test.asm** from the course web page. Open the program in the MARS simulator and go to the execute view (shown below). In the **Code** column, we have the machine code for the instructions. Run the program and convince yourself of its behavior.



The screenshot shows the MARS simulator's 'Text Segment' window. It has 'Edit' and 'Execute' buttons at the top right. Below is a table with columns: Bkpt, Address, Code, Basic, and Source. The table contains 10 rows of assembly code. The last row, at address 0x00400018, is highlighted in yellow.

Bkpt	Address	Code	Basic	Source
<input type="checkbox"/>	0x00400000	0x20040004	addi \$4,\$0,0x00000004	4: addi \$a0,\$0,4
<input type="checkbox"/>	0x00400004	0x20820002	addi \$2,\$4,0x00000002	5: addi \$v0,\$a0,2
<input type="checkbox"/>	0x00400008	0x00441020	add \$2,\$2,\$4	6: add \$v0,\$v0,\$a0
<input type="checkbox"/>	0x0040000c	0x10440002	beq \$2,\$4,0x00000002	7: loop: beq \$v0,\$a0,done
<input type="checkbox"/>	0x00400010	0x2042ffff	addi \$2,\$2,0xffffffff	8: addi \$v0,\$v0,-3
<input type="checkbox"/>	0x00400014	0x1000ffff	beq \$0,\$0,0xffffffff	9: beq \$0,\$0,loop
<input type="checkbox"/>	0x00400018	0x00000020	add \$0,\$0,\$0	10: done: add \$0,\$0,\$0

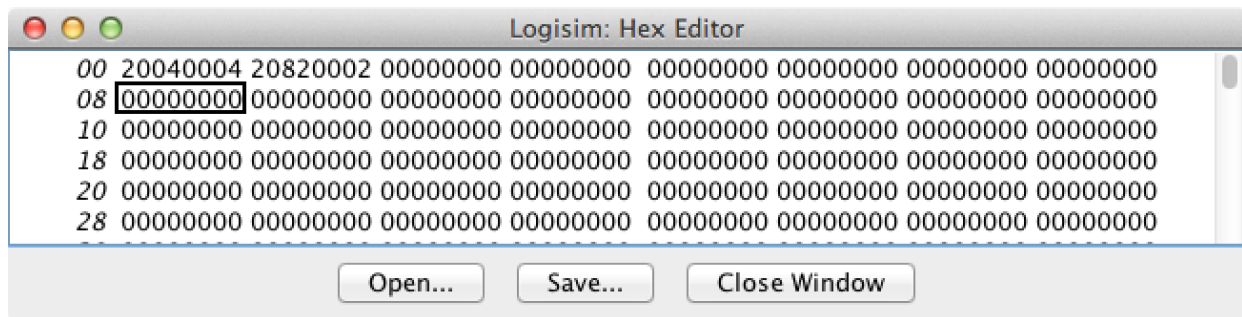2. Enter the machine code for the two first instructions in the ROM memory (the two first **addi** instructions). Before you add the instructions, right click on the component and select "Clear contents". After that you have added the instructions, the edit view should then look like this:



NOTE: you might need to save the content to a file and then load it again to be able to update the memory in the component.

3. Add the **RegisterFile** and the **ALU** components. See the course book and lecture 9 for details about how you implement an immediate instruction. Note that the address width is 3 bits for the **RegisterFile**, which means that you should only use the 3 least significant bits of the MIPS addresses after decoding. To select bits, use the **Bit Selector** component (can be found in the Plexer library folder). In the circuit **Tests**, there are two examples that shows how the Bit selector component can be used. You probably need to play with these examples to understand how it works.
4. Attach the data path to the relevant control signals of the control unit. Do not forget to feed the instruction into the control unit.
5. Test that the execution sequence of the 2 instructions works as expected. You may need to add a few output components to see what happens in the circuit.

#### Task 4.3: Implementing the add instruction (R-type).

1. Open file **test.asm** again in MARS and enter the three first instructions to the ROM component (including the 3<sup>rd</sup> instruction that is an **add**-instruction).
2. Implement the necessary logic for the **add** instruction in the data path. Note that you need to add two multiplexors. Connect these multiplexors to the right control signals.
3. Test that the sequence of two **addi** and one **add** instruction work correctly.

#### Task 4.4: Implementing the beq instruction.

1. Add the logic for the **beq**-instruction. Connect the relevant control signals.
2. Implement the rest of the test program test.asm into the ROM. Initialize the PC to 0x14 and check that the jump is performed.

#### Questions for Assignment 4

These questions are useful to prepare yourself for the oral examination. However, at the examination, the teacher may choose to ask questions that are not on this list.

- Explain how the bit selection works for the alternatives that are controlled by the **RegDst** control signal. Which instructions are using what logic and why?
- Explain how the **beq** instruction is implement, how the address is calculated, and how the signals are controlled by the control unit.

## Assignment 5: Factorial Function in Assembler

In this task, you should develop a small MIPS assembly program and execute it on your new processor.

### Task 5.1

Open the MARS simulator and implement an assembly program that computes the factorial number  $n!$ , where  $n$  is a input parameter. The program has the following requirements:

- Only three instructions are allowed to be used: **add**, **addi**, and **beq**.
- Only registers with numbers 0 to 7 are allowed to be used. That is, you are allowed to use \$0, \$at, \$v0, \$v1, \$a0, \$a1, \$a2, and \$a3.
- The input value should be given in \$a0. That is, the first instruction should assign \$a0 to value  $n$ .
- The final result should be stored in \$v0.
- At the end of the program, implement a “stop” loop, i.e., a loop that jumps to itself forever.

Note that you do not have a **mul** operation available. Hence, you should simply implement the mul operation by performing a loop with **add** instructions. This is not the fastest implementation, but it is good enough for testing your processor!

### Task 5.2

In the MARS simulator, test that the program works for at least  $0!$ ,  $3!$ , and  $8!$ .

### Task 5.3

Move the machine code of the complete program into the ROM memory of your processor. Test that your processor gives the correct result for at least  $0!$ ,  $3!$ , and  $8!$ .

Some advice: You can easily move your machine code from the MARS simulator into the ROM memory in Logisim.

1. In MARS, assemble the program.
2. Choose "Dump Memory..." from the File menu in MARS.
3. In the "Dump Memory To File" dialog window, set "Dump Format" to "Hexadecimal Text".
4. Click "Dump To File..." and save the file on your system as a .txt file such as, "mips1.txt".
5. Use a plain text editor, such as *Notepad* or *gedit*, to open the file ("mips1.txt"), to add a new line at the very beginning of the file with the following contents:  
v2.0 raw
6. Save the file, then load it into Logisim.


On the next page, there is a graphical overview of the procedure.
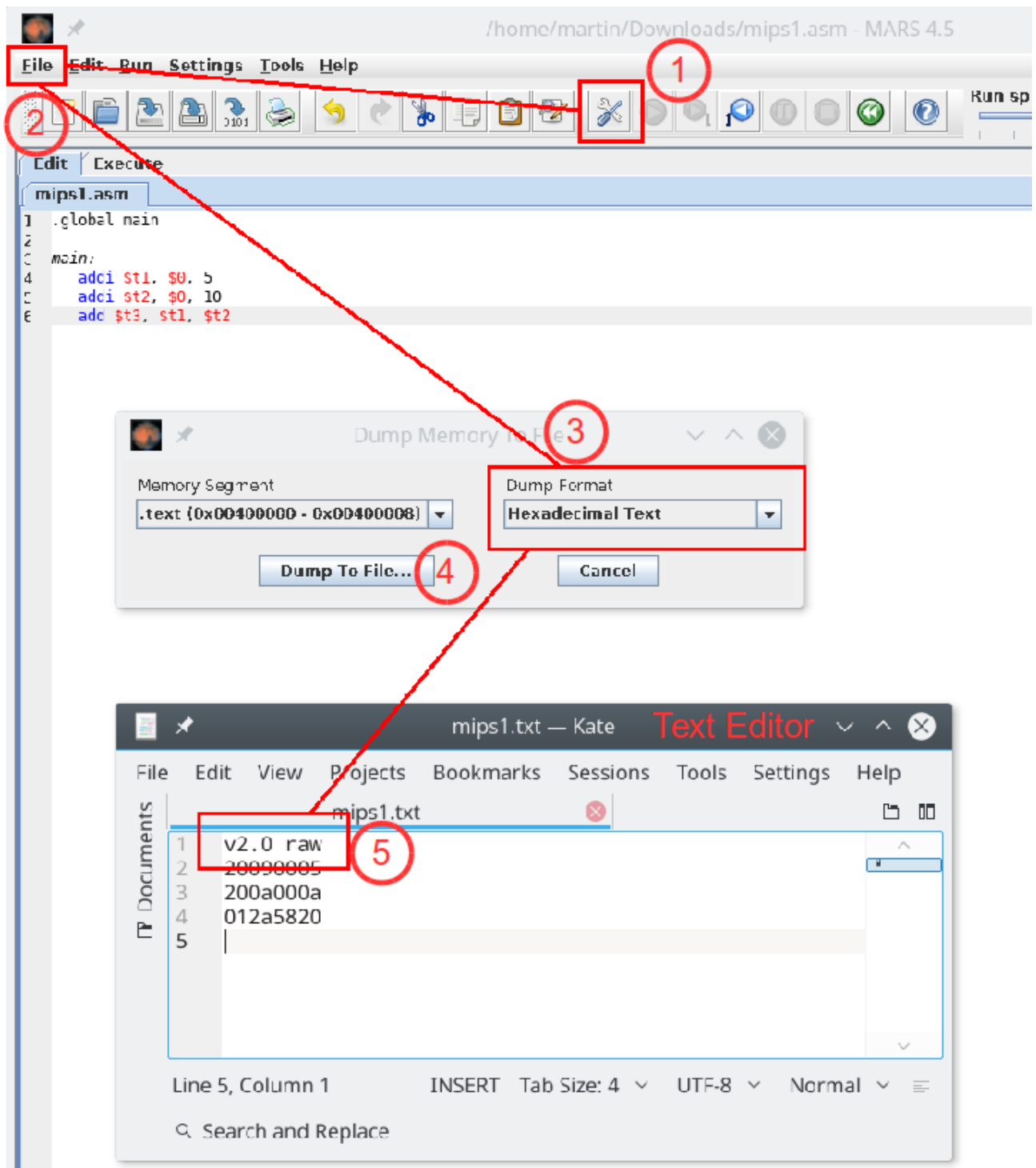
## Questions for Assignment 5

These questions are useful to prepare yourself for the oral examination. However, at the examination, the teacher may choose to ask questions that are not on this list.

- Show and explain how the factorial function works for arbitrary input value  $n$  (the teaching assistant will give you the value that you should test). Be prepared so that you know how to change the input value easily.
- Explain how you implemented unconditional jumps in your program.





## Assignment 6: Surprise assignment

You will get a surprise assignment at the lab session. We will hand out the surprise assignment directly at the beginning of the lab, presupposed that you have finished all the other assignments. If you have not received the surprise assignment, please ask the teaching assistant for the assignment paper.

## ***Revision history***

**2016-08-24:** Added a requirement to Assignment 1: the Subtractor component must not be used.

**2016-01-14:** First published version for Fall, 2016.

**2017-01-17:** Added instructions on how to move machine code from MARS into Logisim.